

ECE 3421 – VLSI Design and Simulation, Spring 2013

Lab Assignment 3 Design and Simulation of a 2-input NOR Gate

The figure 1 shows the logic diagram for a NOR gate.

1. Design a schematic for this circuit in cadence using $W_n = W_p = 2\mu\text{m}$, and $L = 0.6\mu\text{m}$ for both NMOS and PMOS transistors.
2. Make a symbol for this circuit.
3. To test your circuit, plot the input output characteristics.

 


Figure 1: A two input NOR gate.

Assignment

1. Create a schematic for the above NOR gate in cadence.
2. Turn in the Input/output waveform showing all possible input combinations of A & B.
3. What is the worst-case propagation delay and for which input combination? Why do propagation delays vary for different input combinations?
4. Ideally, how fast can this gate can be driven with a load of 1pF capacitor? Show the output waveform of this case. (Hint: The output needs to reach a stable value after each transition.)